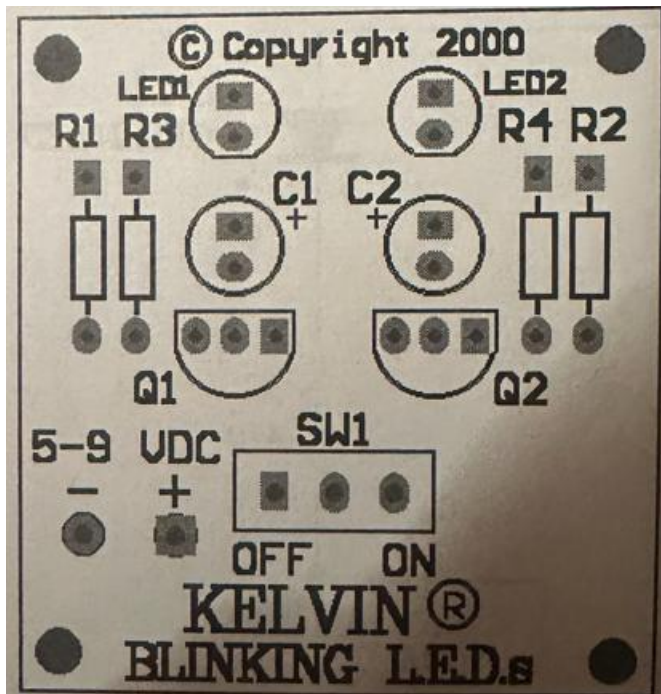


Schematic of Blinking LED Circuit:



Parts of Blinking LED Circuit:

Part reference(s)	Part value	Kelvin part number
Q1,Q2	2N3904 Transistor	630117
LED1	Red LED	260020
LED2	Green LED	260027
R1,R2	470 $\frac{1}{4}$ Watt Resistor	010103
R3,R4	220K $\frac{1}{4}$ Watt Resistor	010060
C1,C2	1 $\mu$ F/50V Capacitor	180012
SW1	SPST Slide switch	270099
BAT	Battery connector	220017

Picture of Blinking LED Circuit:

